

# Digital Logic Design : Sequential Circuit



Z. Jerry Shi

Department of Computer Science and Engineering  
University of Connecticut

Based on materials from Computer Organization: the Hardware/Software Interface by  
D. Patterson and J. Hennessy

# Appendix A

“history” of Input ??

- Clock
- Memory elements
  - D Flip-flops, registers, register file
- State machines and timing

G	M	K	unit	m	u	n
$10^9$	$10^6$	$10^3$	$10^0$	$10^{-3}$	$10^{-6}$	$10^{-9}$

Reading: Sections A.7 - A.11


# Combinational versus sequential

---

Two types of circuit:

- **Combinational circuit**: the outputs depend on the **current** input values
- **Sequential circuit**: the outputs also depend on the **history** of inputs
  - Two identical sequential circuits may produce different outputs even if their current inputs are the same

# Clock

 


- A clock signal oscillates between high and low values
- The clock period is the time for one full cycle  $\approx 0.2$ 
  - Also called **clock cycle time** (sec)
  - The **clock rate** is the reciprocal of the cycle time  $\approx$  frequency (Hz)

If the clock cycle time is 1 ns, the clock rate is 1 GHz.

If the clock rate is 2 GHz, the clock cycle time is 0.5ns.

$$\frac{1}{2\text{GHz}} = 0.5\text{ns}$$

 

# Question

---

If a processor runs at 200 MHz, what is the clock cycle time in ns?

Round to the nearest integer.


$$\frac{1}{200\text{MHz}} = 0.005\mu\text{s}$$
$$\triangleq 5\text{ns}$$

Why cannot the <sup>High Temp!!</sup> processor run at higher clock rates?

We are going to see why.
 
# Bistable element


- A bistable element has two states: Q is 0 or 1
- The simplest sequential circuit to remember something
  - Need memory to remember **history** in sequential circuit



Based on bistable element, we build flip-flops, which are easier to use
 
# D flip-flop, **positive** edge triggered

- D flip-flop stores input D at the trigger, the **rising edge** of C *clock*
  - We can control what and when
  - To store a bit in D flip-flop: set up D, and then make C transit from 0 to 1
  - The saved bit does not change until another value is stored




# Timing requirements of D Flip-Flop

**Setup time:** D has to be steady for some time before the edge

**Hold time:** D has to be steady for some time after the edge

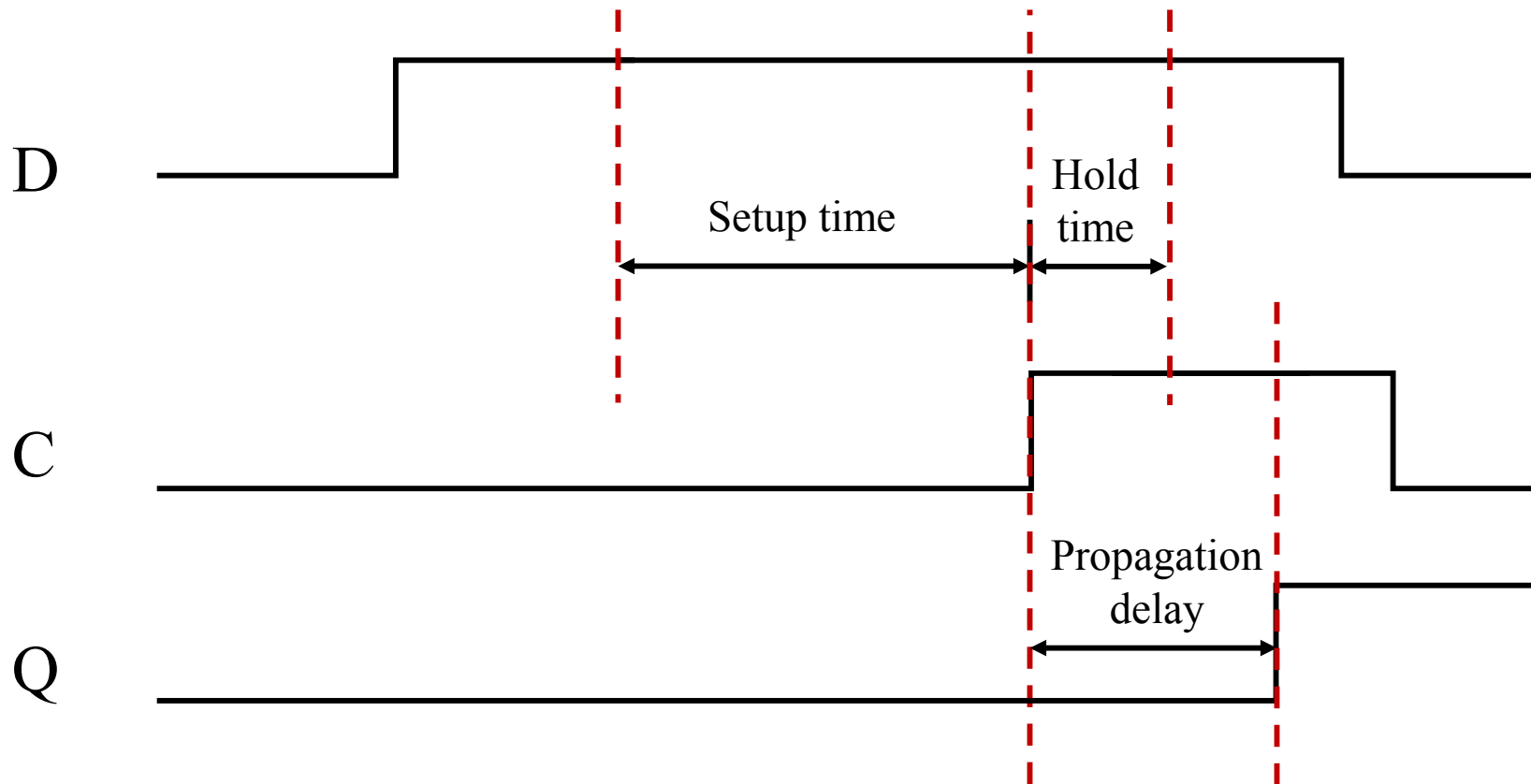**Propagation delay:** Time for input to propagate to output






# Register


(X<sub>0</sub> ~ X<sub>31</sub>)

- Register: a memory element that stores data
  - Can be a D flip-flop, or other kind of flip-flops
- A clock signal determines when to update the data
  - The timing diagram below is for a positive edge-triggered register
  - Update happens when clock changes from 0 to 1
- Data stored in registers are steady until next trigger

if statement

 


if clk  
Q == D

 

 
# Register with write control

$RISC-V$   $\begin{cases} \text{write } (Rd) \\ \text{read } (Rs1, Rs2) \end{cases}$


- The register is updated with D on clock edge **only when write control input is 1**
  - Otherwise, keep the original value in the register
  - Often, the Write signal is also called Enable



How would you add the Write control?

 


 if  $write = 1$  &  $clk \uparrow$   
 $Q \leftarrow D$


 
# Multibit Register

- But that's only 1 bit
- How would you build a 32-bit register?




We could use Write to block clock.  
It is better to use Write to select one of D and Q

# 32-bit Register

- An array of 1-bit registers
  - Controlled by the same clock




Remember RISC-V has 32 registers?

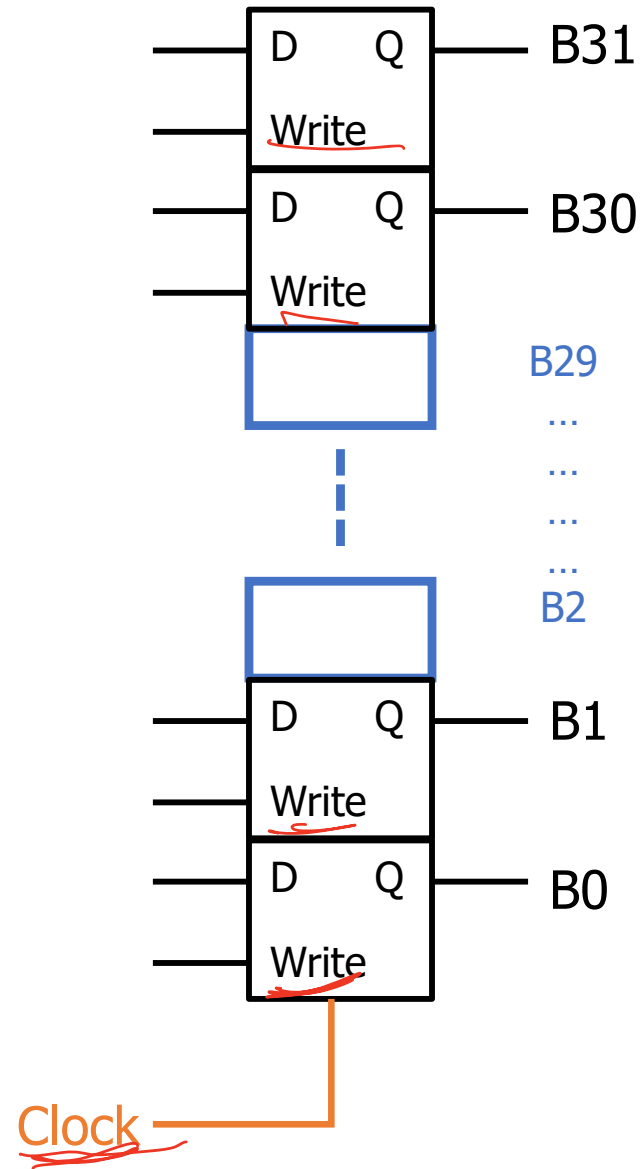
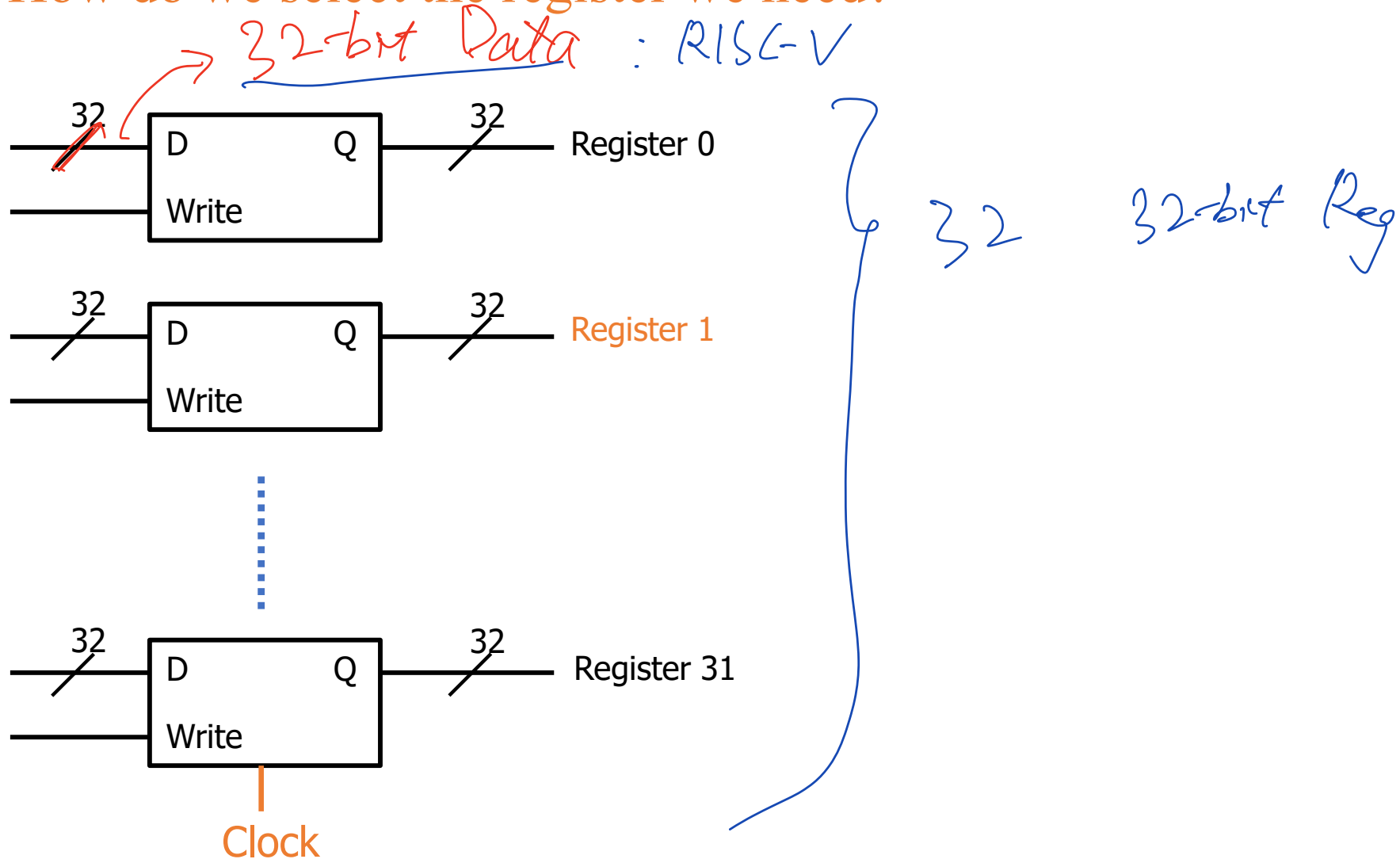
# Register File


- The register file has 32 32-bit Registers
- How do we select the register we need?



# Inside the RF: Read ports

$RS1 \quad RS2 \rightarrow \text{add } x1, x30, x31$

- Two MUXes for Two read ports

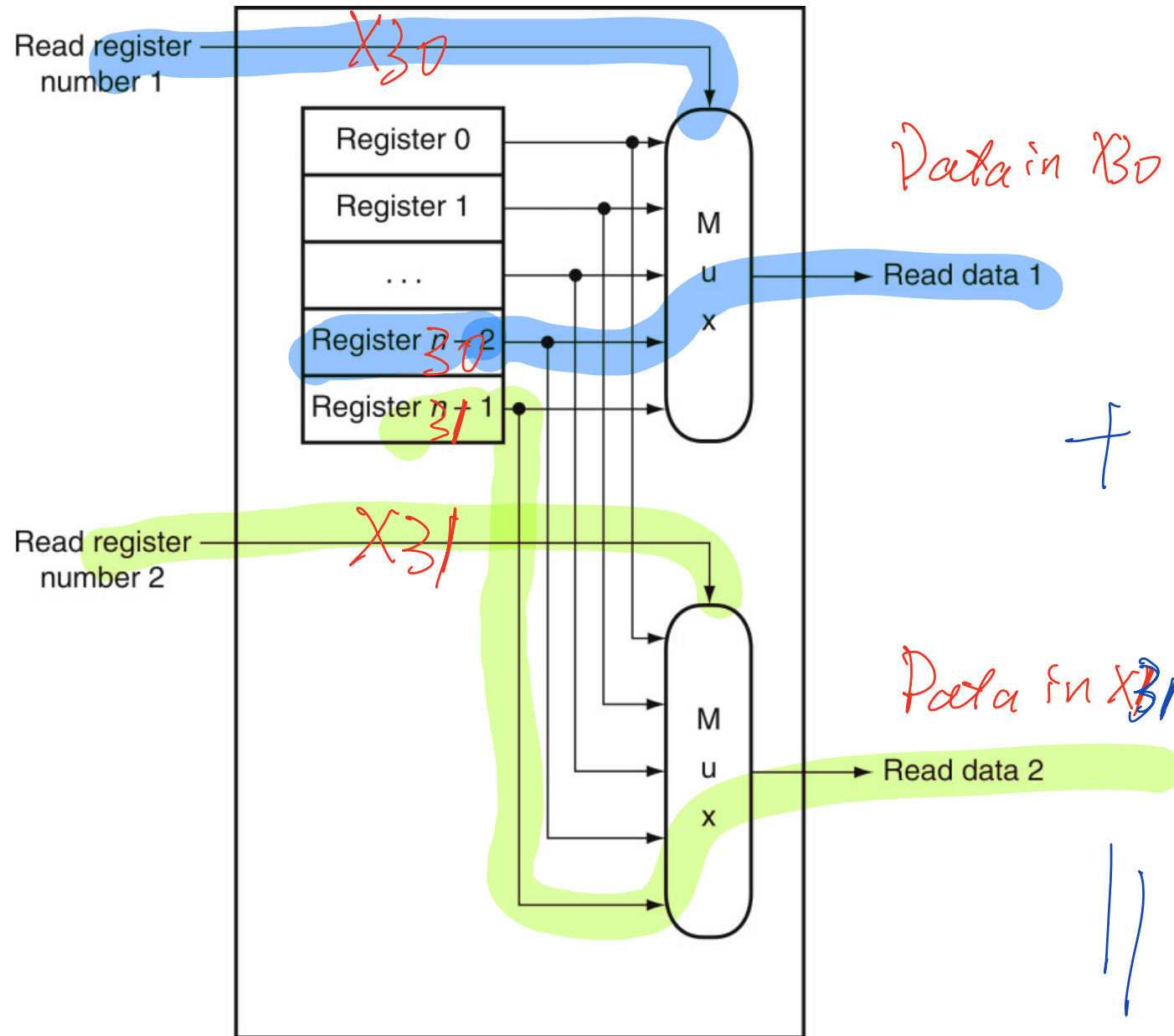

How do we select the register to write?

# Inside the RF: Write port

Data in X31  
Data in X30 = Temp

Write goes to AND gates


Register number goes into a decoder, which activates only one register

Register Data are sent to all registers

Data to be stored

Register data

Clock

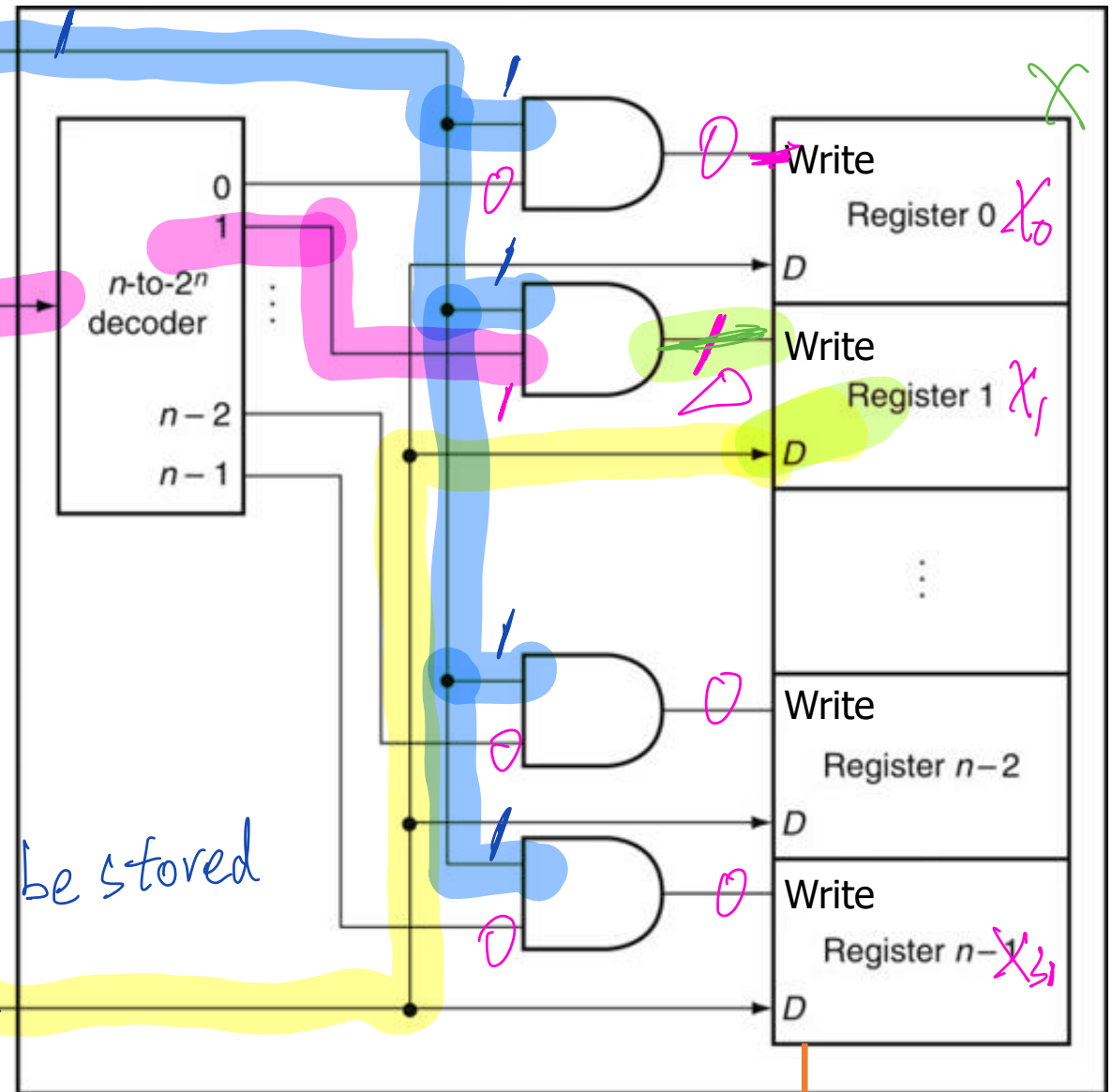

# Register File

- Register File (RF) has a collection of registers
- RISC-V RF has 32 32-bit registers
  - Two read ports: can read two registers at the same time
  - One write port
    - Set **Write** to 0 if the instruction does not write to a register

*beg X*

*addi ?*


## Read

Set read register numbers  
Wait for data to be ready

## Write

Set write register and write data  
Set **Write** to 1  
Wait for clock to change

**Clock?** Not shown.

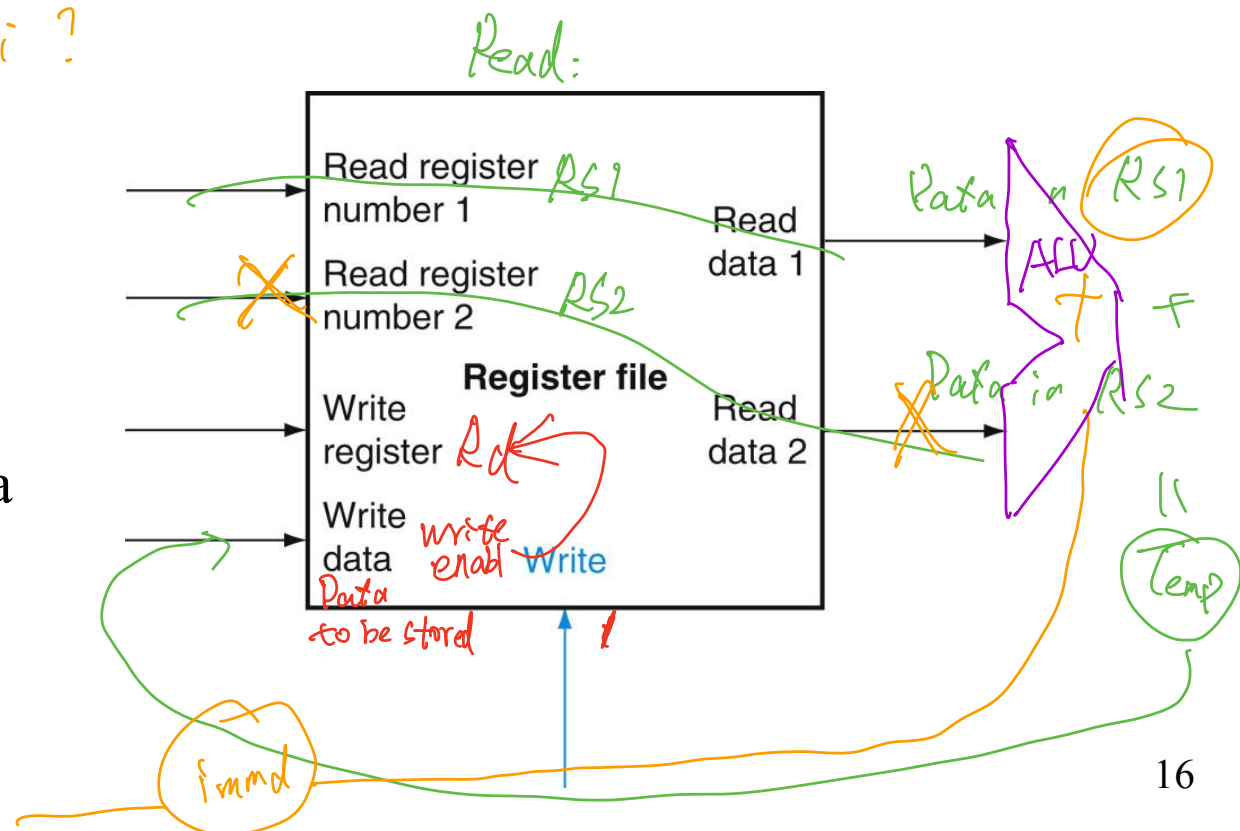



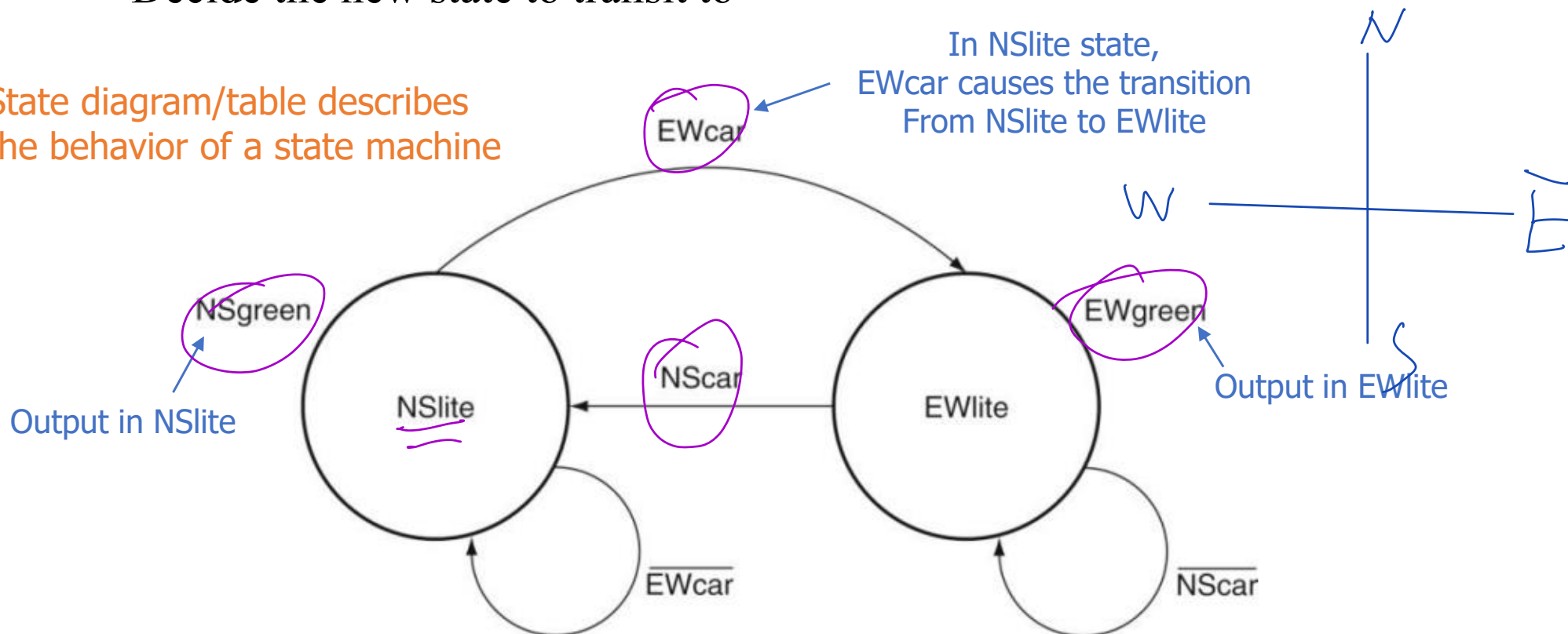
# State Machine


- The circuit has multiple states
  - A state is a summary of previous inputs
- The circuit does two things, depending on current state and input
  - Generate output,
  - Decide the new state to transit to

State diagram/table describes the behavior of a state machine


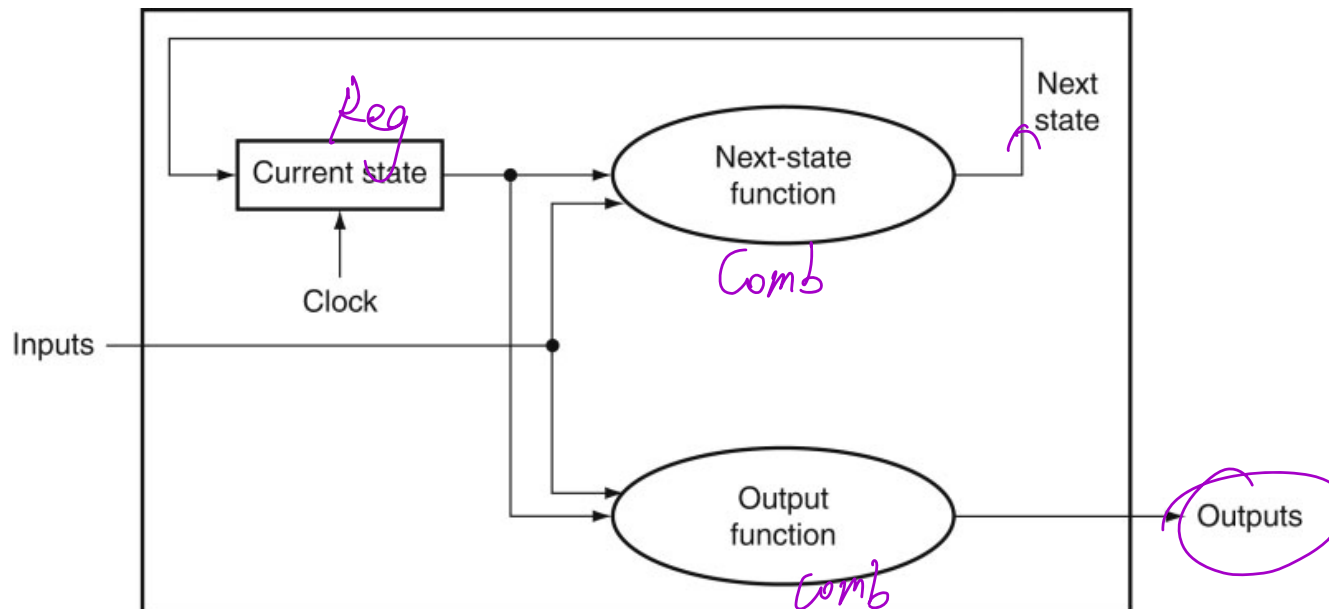
# Components in a State Machine


- A state machine consists of
  - Memory elements that keep the state
    - Commonly use edge-triggered memory elements
    - All bits are updated **at the clock edges** and kept steady during the cycle
  - Two combinational functions
    - One generates output
    - One generates the next-state, which will be saved in memory elements when triggered



## Example: a 16-bit Accumulator


- Add an input number to the existing value in the register
  - If In is 1, the accumulator works as a counter

Identify the following:

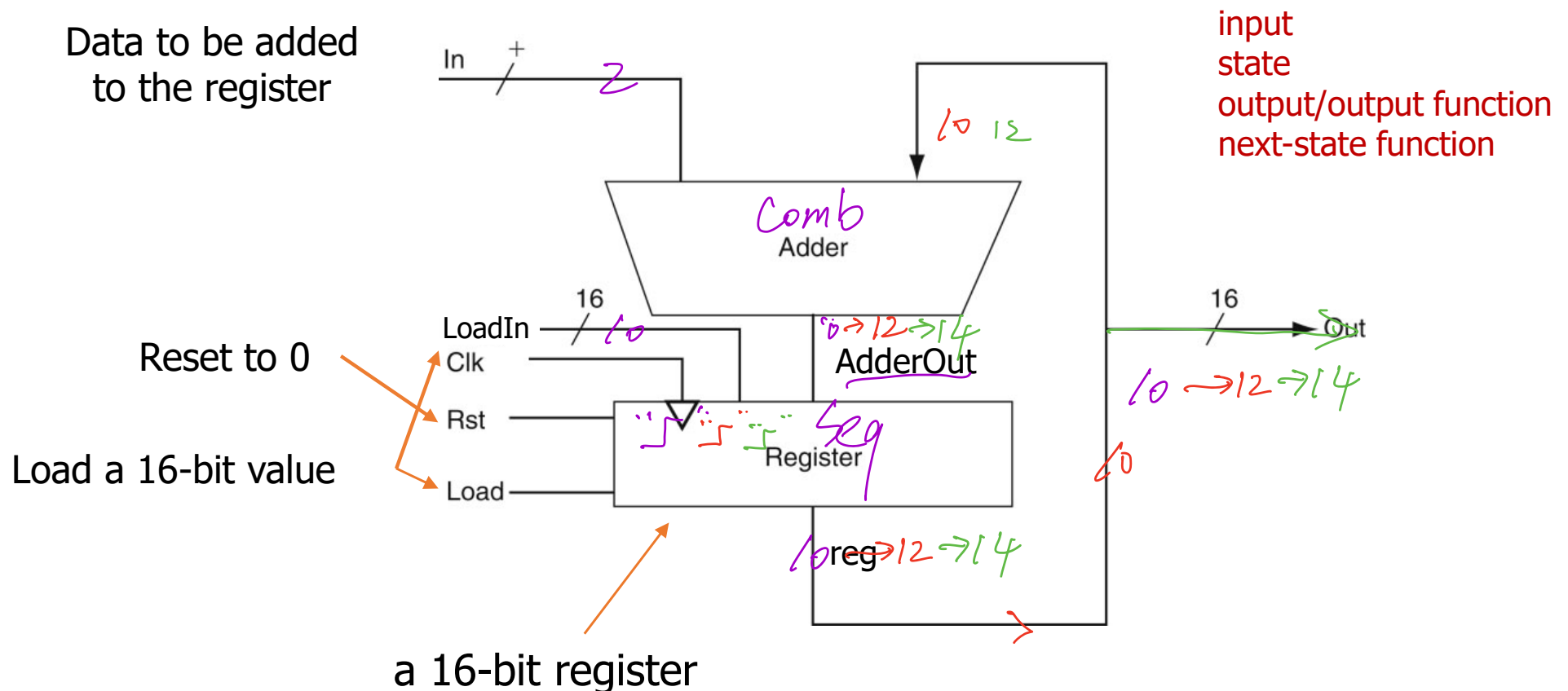

 
# What is happening in a cycle

- Between clock edges:
  - New state is stored in the state elements
  - Combinational logic computes
  - State for next cycle is presented at the input of the state elements
- The clock cycle must be long enough to complete all work


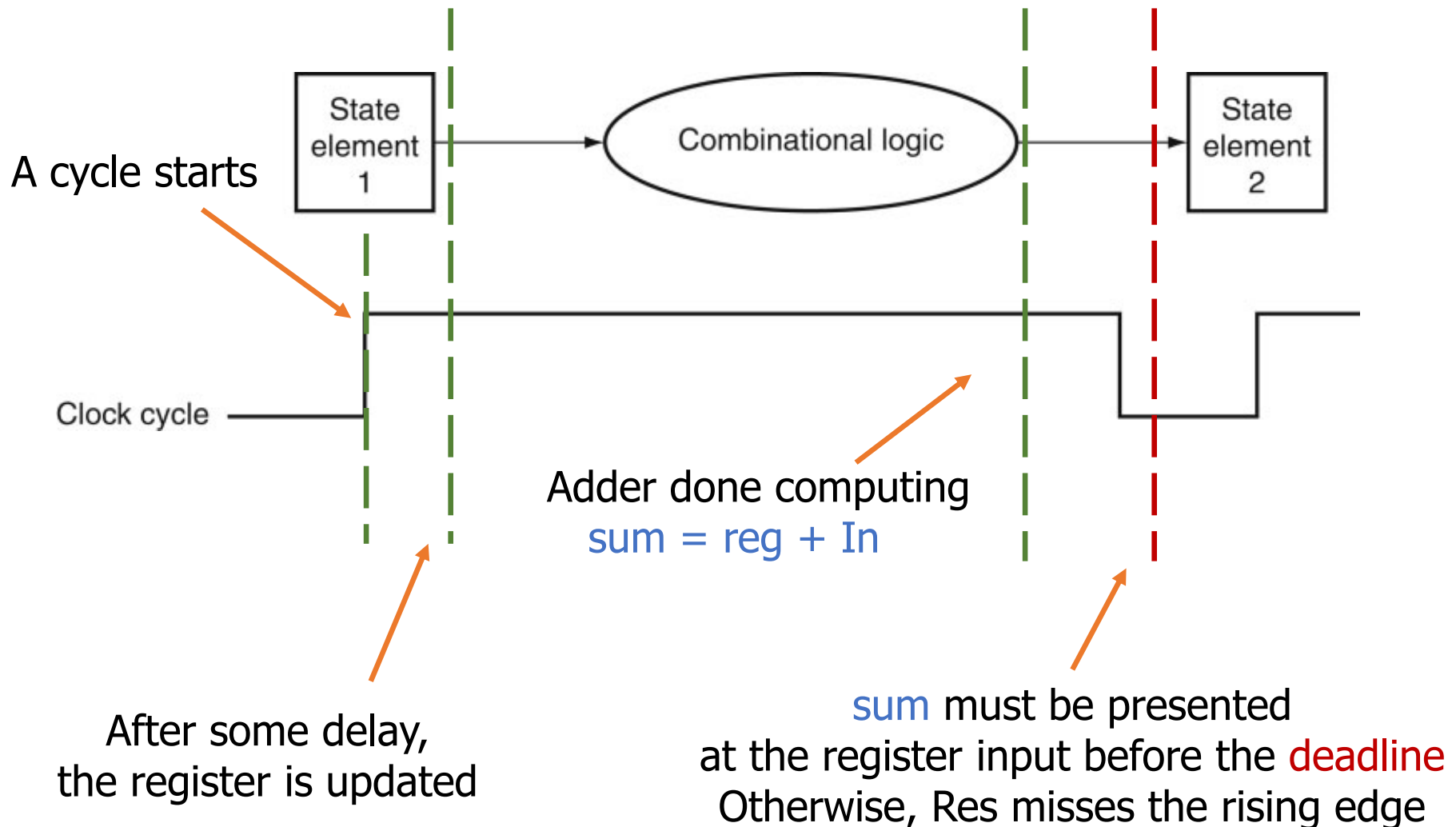
# Example of a 16-bit Accumulator


- What happens in a cycle (when accumulating)?


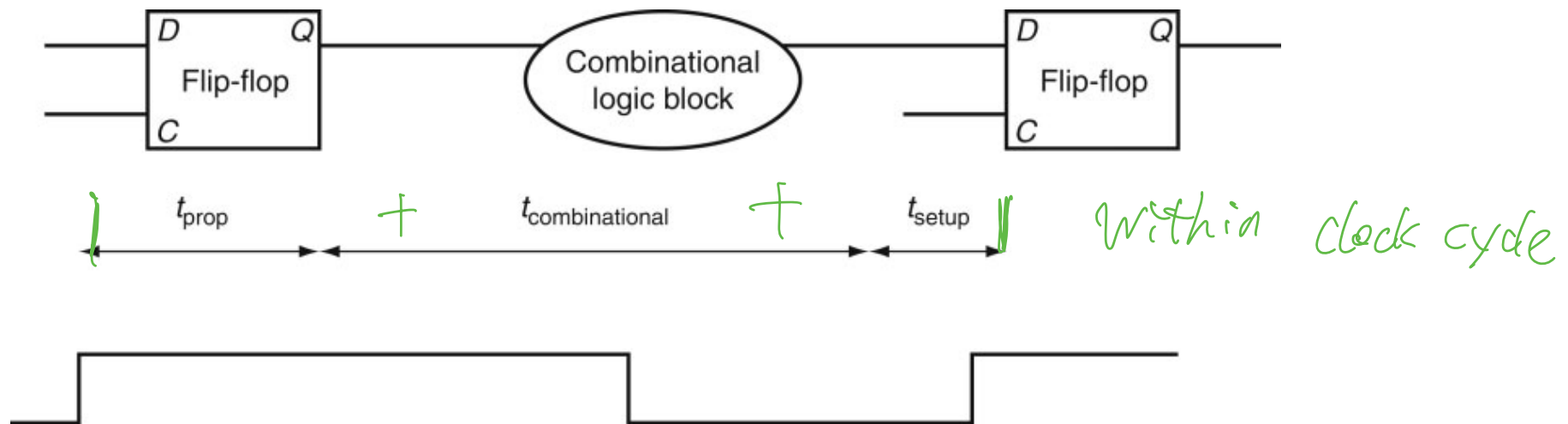
# Clock Rate

The clock cycle must be longer than the sum of the following delays

- $t_{\text{prop}}$  : The time for a flip-flop to propagate input to the output;
- $t_{\text{combinational}}$  : The time for the combinational logic to work;
- $t_{\text{setup}}$  : New state must arrive early enough to meet the setup requirement



Identify the delays on the previous slides.

Where is the hold time?

# Question


The setup time and hold time of the register is 2ns and 1ns, respectively

The propagation delay of the register is 3 ns.

The propagation delay of the adder is 10 ns.

**What is the fastest clock rate in MHz the accumulator can work at?**

Truncate to the nearest integer.

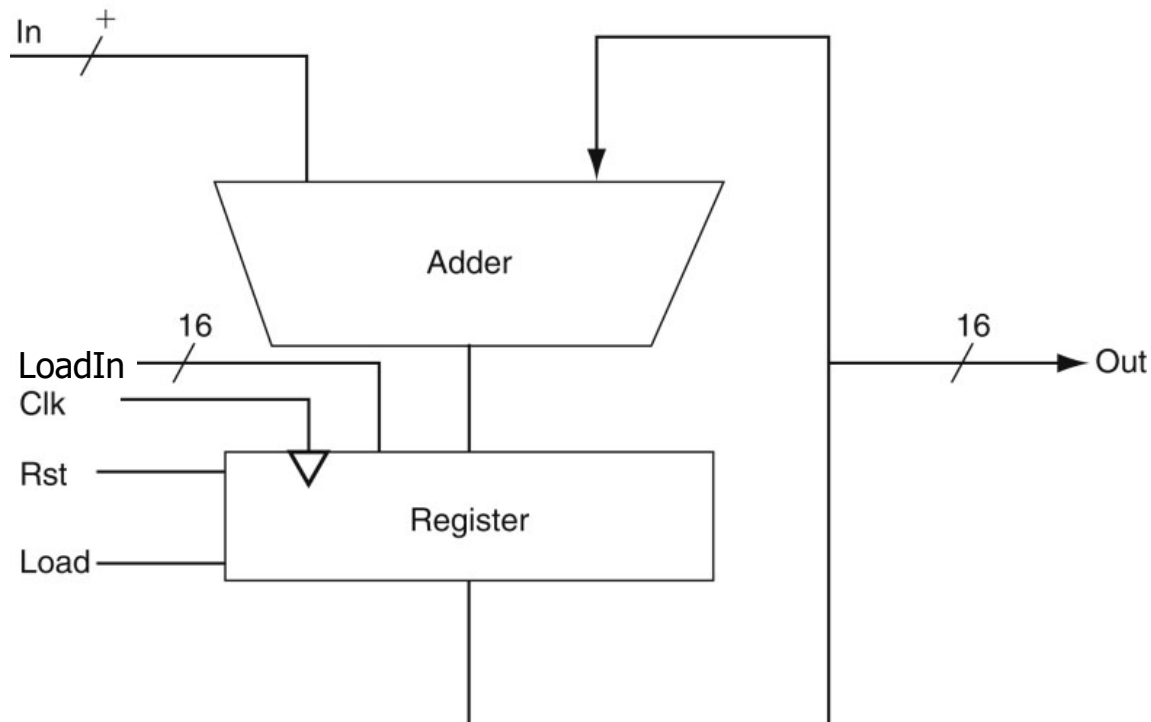

# Solutions

---

The clock cycle must be longer than the sum of the following delays

$t_{\text{prop}}$  : The time for a flip-flop to propagate input to the output;

$t_{\text{combinational}}$  : The time for the combinational logic to work;

$t_{\text{setup}}$  : New state must arrive early enough to meet the setup requirement

$$\text{Clock cycle time} \geq t_{\text{prop}} + t_{\text{combinational}} + t_{\text{setup}} = 3 + 10 + 2 = 15\text{ns}$$

$$\text{Clock rate} \leq 1 / 15\text{ns} = 0.0667 \text{ GHz} = 66 \text{ MHz}$$



# Design of memory

---

- Memory provides a large storage for processors
- Conceptually, memory is just a large register file, but it is very large, which changes many design decisions *access is slow*
  - Each cell (for a bit) must be small and cheap
    - Not using flip-flops
  - Memory is slow (very slow)
    - Pick one word out of 32 vs one out of 1 billion
    - Memory has its own clock
  - Memory consumes a lot of energy


# Memory vs. RF

- Read

- Set Address and MemRead (to 1), and wait
- Get the data from Read data

- Write

 - Set Address, Write data, and MemWrite (to 1), and wait




MemWrite and MemRead should not be 1 at the same time
 
# Example: Shift Register

- Registers that can shift bits to right (or left)
  - A simple state machine

For example: 4-bit shift register (shift right)




	Cycle	S	B3	B2	B1	B0
→	0	0	1	0	1	1
→	1	1	0	1	0	1
→	2	1	1	0	1	0
	...					

# Example: 4-bit shift register
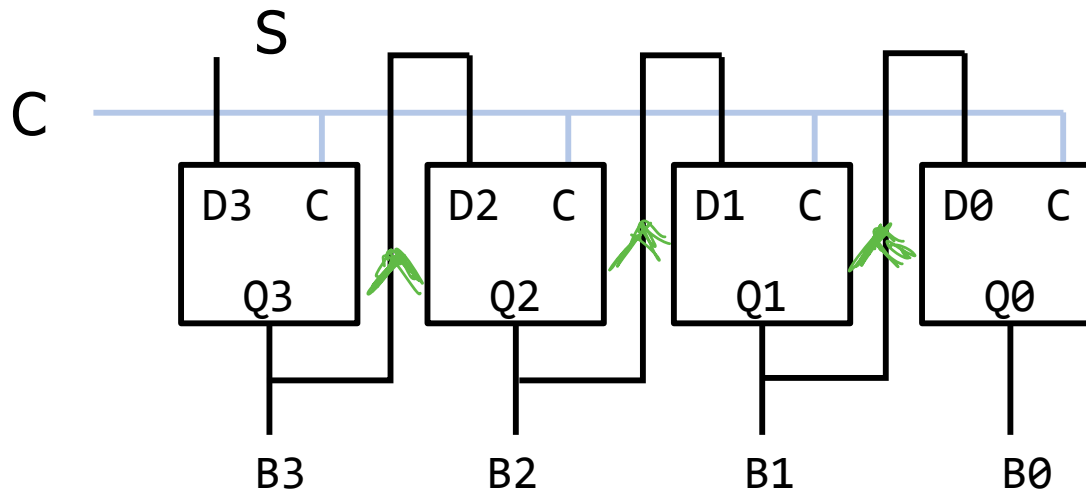
## Shift right

Bits to be stored in the register in the next cycle: (S, B3, B2, B1)

- S is connected to D3 because we want S to be stored in bit 3 of the register
- Similarly, B3 is connected to D2, B2 to D1, and B1 to D0



How about shift left?

# Clock skew


XX (not in exam)

- Clock arrives at memory elements at different times
  - Also called **timing skew**
- Clock cycle time needs to include the clock skew
  - However, we don't consider it in this course


 
# D flip-flop, <sup>Falling edge</sup> **negative** edge triggered

- Negative edge triggered D flip-flop stores D at the **falling edge**



# Register with reset and enable in HDL

---

In Verilog:

```
always @ (posedge clk or posedge reset)
begin
    if (reset == 1) begin
        q <= 0;
    end else if (enable == 1) begin
        q <= d;
    end
end
```

In MyHDL:

```
@always_seq(clk.posedge, reset=reset)
def seq_reg():
    if enable:
        q.next = d
```

# Truth table in state machine

Assume 3-bit state, 2-bit input, 2-bit output

For each state and input combination, specify what the next state and output are

					Next state			Output	
					S2	S1	S0	Out1	Out0
State 0	{	S2	S1	S0	I1	I0			
		0	0	0	0	0			
		0	0	0	0	1			
		0	0	0	1	0			
State 1	{	0	0	0	0	1			
		0	0	1	0	0			
		0	0	1	0	1			
		0	0	1	1	0			
	{	0	0	1	0	1			
		...							